

BEE Assignment - 2


Q1] Explain Ideal & Practical voltage sources & ideal & practical current sources.

→

1] Ideal Voltage source:-

→

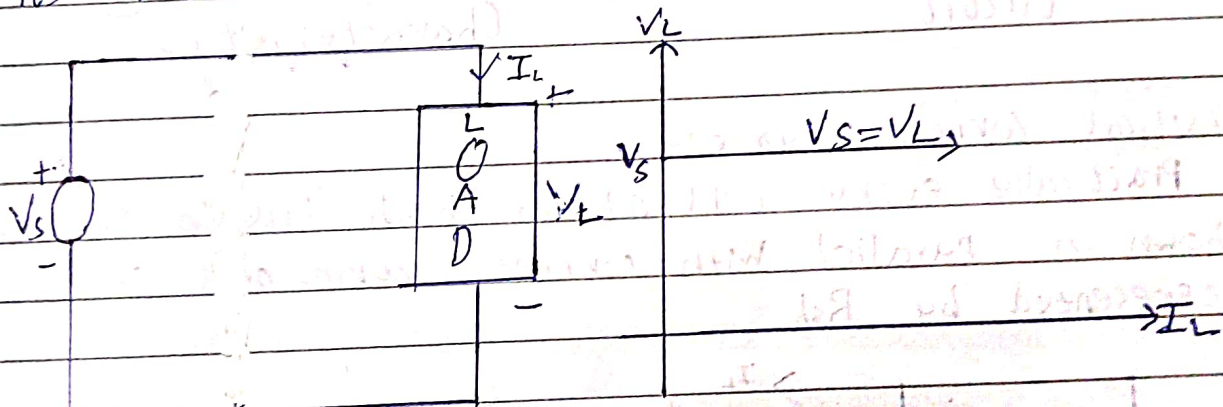An Ideal Voltage source is one which gives constant voltage across its terminal irrespective of current drawn. Symbol for ideal voltage source and its V-I characteristics are shown in fig.




Circuit

Characteristics

2] Practical Voltage source

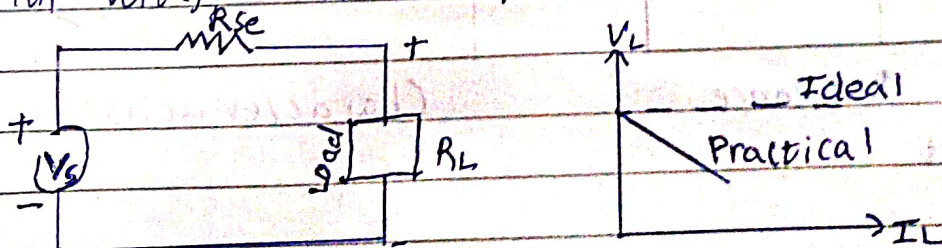Every voltage source has small ^{internal} resistance shown in series with voltage and is represented by R_{sc} as shown in fig




Circuit

Characteristics


3] Ideal current source:-

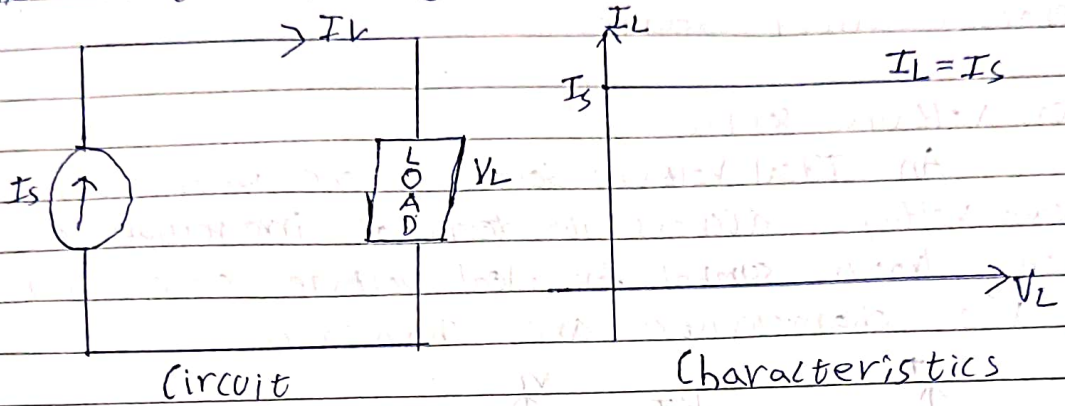Ideal current source is the source which gives constant current at its terminal irrespective of the voltage appearing across its terminal.



4] Practical current source:-

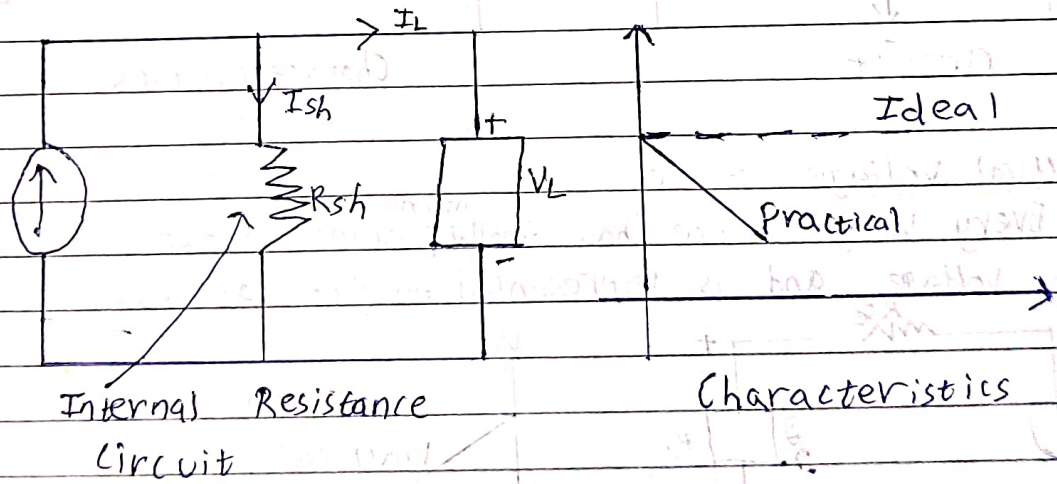Practically every current has high internal resistance, shown in parallel with current source and its represented by R_{sh}



Q2] State & Explain Superposition theorem.

• Statement:-

Superposition theorem states that in any linear bilateral Network containing two or more sources, the current in any element is equal to algebraic sum of current caused by individual source acting alone, while other sources are inoperative.


• Steps to apply Superposition theorem:-

Step 1:- Select a single source acting and short the other voltage sources and open the current sources,

Step 2:- Find the current through or the voltage across the required elements to the source under consideration using a suitable network simplification technique.

Step 3:- Repeat the above two steps for all the sources

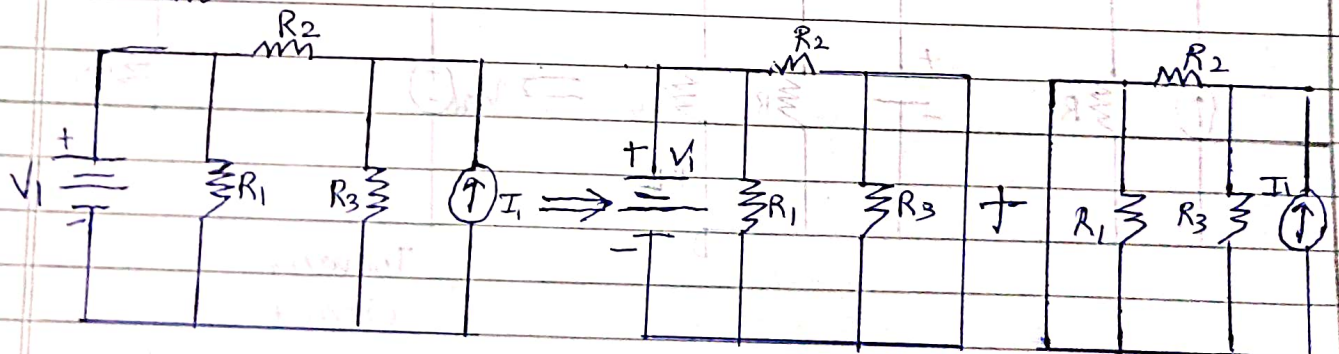Step 4:- Add the individual effects produced by individual sources to obtain the total current in or voltage across the element.



237 State and explain thevenins theorem

• Statement :-

It states that any linear circuit containing several voltage sources and resistors can be simplified to a thevenins equivalent circuit with single voltage source and resistance connected in series with load.

• Steps to apply thevenins theorem:-


Step 1:- Remove the branch the current through which to be obtained.

Step 2:- Calculate the open circuit voltage V_{TH}


Step 3:- Obtain R_{eq} between open circuit

Step 4:- Draw thevenin equivalent circuit and connect the removed branch to find branch current

$$I_L = \frac{V_{TH}}{R_{eq} + R_L}$$

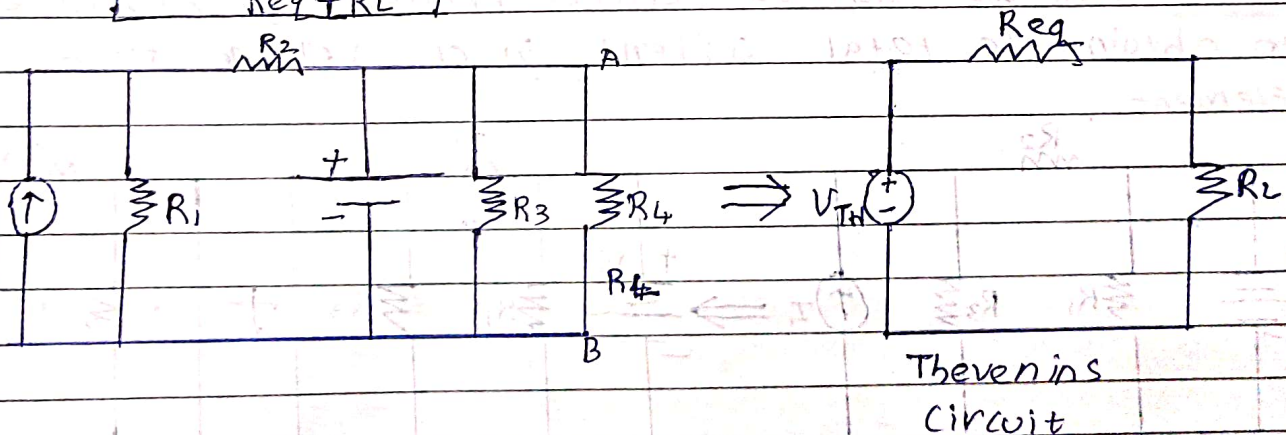

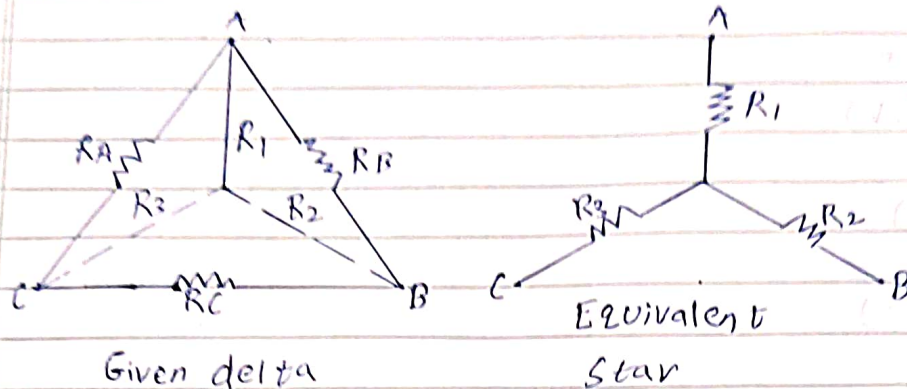Q7 Derive the expression for delta to star conversion



Consider 3 resistances R_A, R_B, R_C connected in Delta shown in figure

$$R_1 = \frac{R_A R_B}{R_A + R_B + R_C}, \quad R_2 = \frac{R_B R_C}{R_A + R_B + R_C}, \quad R_3 = \frac{R_A R_C}{R_A + R_B + R_C}$$

Consider A B

$$R_B \parallel (R_A + R_C)$$

$$\frac{R_B(R_A + R_C)}{R_A + R_B + R_C} \quad \text{--- (1)}$$

Consider B C

$$R_C \parallel (R_B + R_A)$$

$$\frac{R_C(R_A + R_B)}{R_A + R_B + R_C} \quad \text{--- (2)}$$

Consider C A

$$\frac{R_A(R_B + R_C)}{R_A + R_B + R_C} \quad \text{--- (3)}$$

from figure (b)

Consider A + B

$$R_1 + R_2 = (iv)$$

Consider B + C

$$R_2 + R_3 = (v)$$

Consider A + C

$$R_1 + R_3 = (vi)$$

$$R_1 + R_2 = \frac{R_B(R_A + R_C)}{R_A + R_B + R_C} \quad - (vii)$$

$$R_2 + R_3 = \frac{R_C(R_A + R_B)}{R_A + R_B + R_C} \quad - (viii)$$

$$R_1 + R_3 = \frac{R_A(R_B + R_C)}{R_A + R_B + R_C} \quad - (ix)$$

Subtract (vii) - (viii)

$$R_1 - R_3 = \frac{R_B(R_A + R_C) - R_C(R_A + R_B)}{R_A + R_B + R_C} \quad - (x)$$

Add (ix) + (x)


$$2R_1 = \frac{R_A R_B + \cancel{R_A R_C} + \cancel{R_B R_C} + R_B R_A - \cancel{R_C R_A} - \cancel{R_C R_B}}{R_A + R_B + R_C}$$

$$R_1 = \frac{R_A R_B}{R_A + R_B + R_C}$$

Similarly

$$R_2 = \frac{R_B R_C}{R_A + R_B + R_C}, \quad R_3 = \frac{R_A R_C}{R_A + R_B + R_C}$$

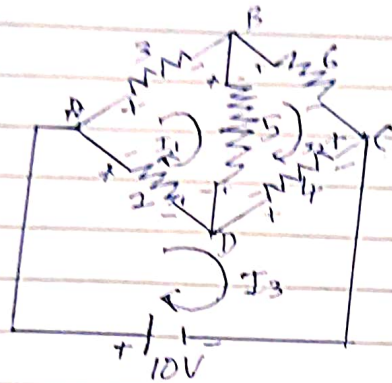Q5] Using Kirchhoff's law calculate current flowing through R_B



For Loop 1

$$\begin{aligned} -3I_1 - 5(I_1 - I_2) - 2(I_1 - I_3) &= 0 \\ -3I_1 - 5I_1 + 5I_2 - 2I_1 + 2I_3 &= 0 \\ -10I_1 + 5I_2 + 2I_3 &= 0 \quad \text{--- (1)} \end{aligned}$$

For loop 2

$$\begin{aligned} -6I_2 - 4(I_2 - I_3) - 5(I_2 - I_1) &= 0 \\ -6I_2 - 4I_2 + 4I_3 - 5I_2 + 5I_1 &= 0 \\ 5I_1 - 15I_2 + 4I_3 &= 0 \quad \text{--- (2)} \end{aligned}$$

For loop 3


$$\begin{aligned} -2(I_3 - I_1) - 4(I_3 - I_2) + 10 &= 0 \\ -2I_3 + 2I_1 - 4I_3 + 4I_2 + 10 &= 0 \\ 2I_1 + 4I_2 - 6I_3 &= -10 \quad \text{--- (3)} \end{aligned}$$

From eqn (1), (2) + (3)


$$I_1 = 1.11, \quad I_2 = 1.11, \quad I_3 = 2.77$$

\therefore Current flowing through $R_{BC} = I_2 = \underline{\underline{1.11}}$

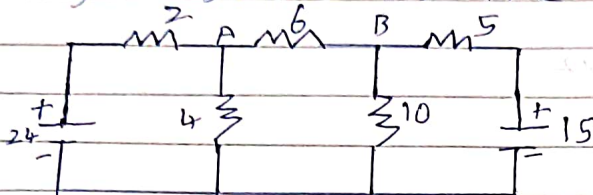Q7] Using thevenins theorem determine value of current flowing through 6Ω resistance



Step 1

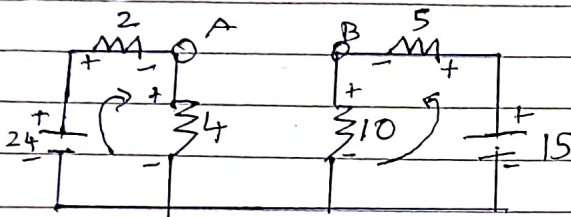

Step 2 :-

$$-2I_1 - 4I_1 + 24 = 0 \quad ; \quad -5I_2 - 10I_2 + 15 = 0$$

$$-6I_1 + 24 = 0$$

$$-15I_2 + 15 = 0$$

$$24 = 6I_1$$

$$15 = 15I_2$$

$$I_1 = 4$$


$$I_2 = 1$$

Trailing path for V_{TH}



$$V_{TH} = 16 - 10 = 6$$

Step 3:- Req

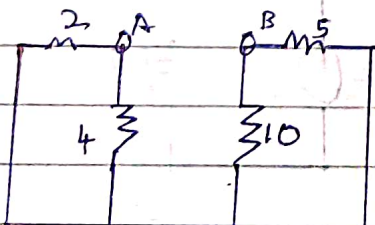


$$4 \parallel 2 + 5 \parallel 10$$

$$\frac{4 \times 2}{4 + 2} + \frac{5 \times 10}{5 + 10}$$

$$1.33 + 3.33 \Rightarrow 4.66$$



Step 4: thevenins circuit

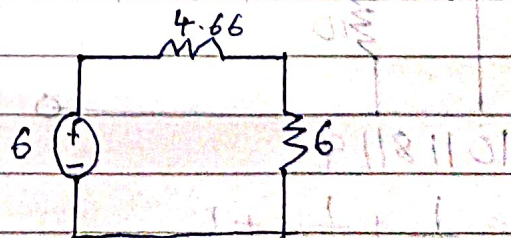

$$I = \frac{6}{4.66 + 6} = 0.56$$

$$4.66 + 6$$

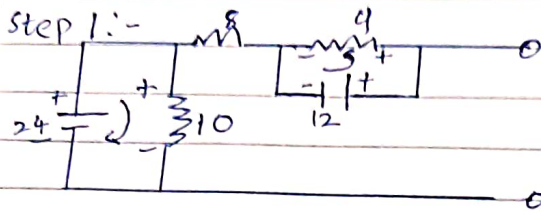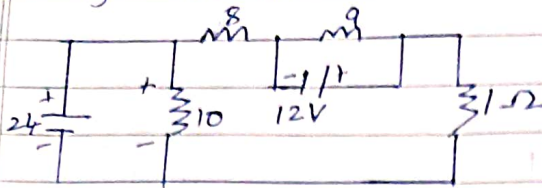Q8] Using Thevenins theorem calculate current in 1-2 resistance




Step 2:-

$$-10I_1 + 24 = 0 \quad ; \quad -9I_2 + 12 = 0$$

$$24 = 10I_1 \quad ; \quad 12 = 9I_2$$


$$I_1 = 2.4 \quad ; \quad I_2 = 1.33$$

Tracing path for V_{TH} -

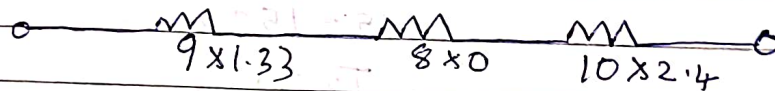

$$V_{TH} = 24 - 12 = 12$$

Step 3:- Req

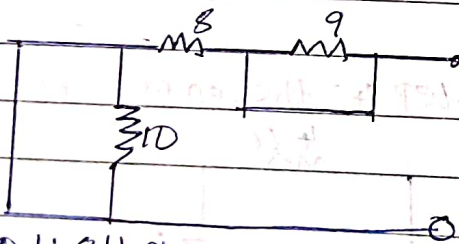


$$10 \parallel 8 \parallel 9$$

$$\frac{1}{R_{eq}} = \frac{1}{10} + \frac{1}{8} + \frac{1}{9}$$

$$\frac{1}{R_{eq}} = 0.336 \Rightarrow R_{eq} = 2.976$$

Step 4:- thevenins circuit

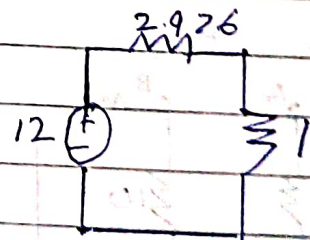

$$I_L V_{TH} = 12 = 3.018 / 3.976$$